

Consider a parallel circuit with  $n$  resistors, with resistance values  $R_1, R_2 \dots R_n$ . The combined resistance will be:

$$\sum R = (R_1^{-1} + R_2^{-1} + \dots + R_n^{-1})^{-1}$$